

Electronics-I

Quiz 3

Max Marks. 10

Name:

Roll No:

Section

All questions are compulsory and use the space on this sheet with proper planning.

Q.1: Implement the complement of function $F(A, B, C, D) = \Sigma (0, 2, 3, 4, 5, 8, 10, 12)$ using minimum number of 2-input NOR gates. [3]

Q.2: Implement a full adder using two 4x1 multiplexers. [3]

Q.3: A PN flip-flop has 2 inputs P and N and output Q. It performs four operations: reset the output to 0, no change in output, complement the output, and set the output to 1, when inputs P and N are 00, 01, 10, and 11, respectively. [4]

(a) Tabulate the characteristic table.

(b) Derive the characteristic equation


Ans 1 $F(A, B, C, D) = \Sigma (0, 2, 3, 4, 5, 8, 10, 12)$

$\Rightarrow \bar{F} = \Pi (0, 2, 3, 4, 5, 8, 10, 12)$

AB \ CD	00	01	11	10
00	0	1	0	0
01	0	0	1	1
11	0	1	1	1
10	0	1	1	0

[1]

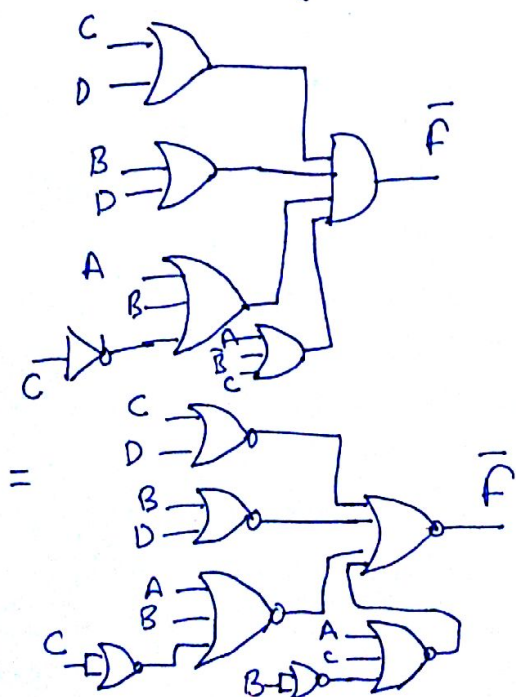$\bar{F} = (C+D)(B+D)(A+B+\bar{C})$
 $(A+\bar{B}+C)$




[2]


Ans - 2.

a	b	C_{in}	S	Count
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

[1]

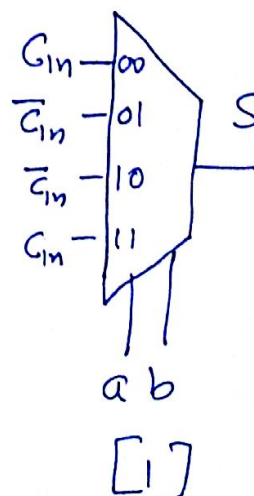

[1]

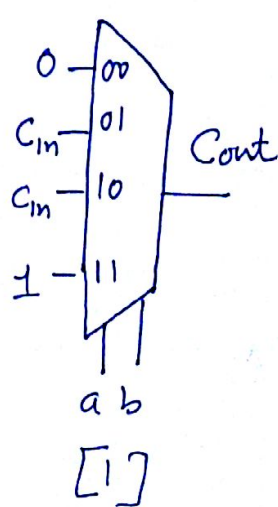

[1]

Ans-3

[2]

P	N	Q(t)	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Q(t+1)

P \ N Q(t)	00	01	11	10
0			1	
1	1		1	1

$$Q(t+1) = P\overline{Q(t)} + NQ(t)$$

[2]
